



**MANIPAL INSTITUTE OF TECHNOLOGY**  
**MANIPAL**  
 (A constituent unit of MAHE, Manipal)

**DEPARTMENT OF ELECTRICAL & ELECTRONICS ENGINEERING**

**ELE 1051: BASIC ELECTRICAL TECHNOLOGY**

**End Semester Examination: Scheme of Evaluation**

1 A. Resistance between the terminals A & B in the circuit shown in Fig. 1 A is

3M



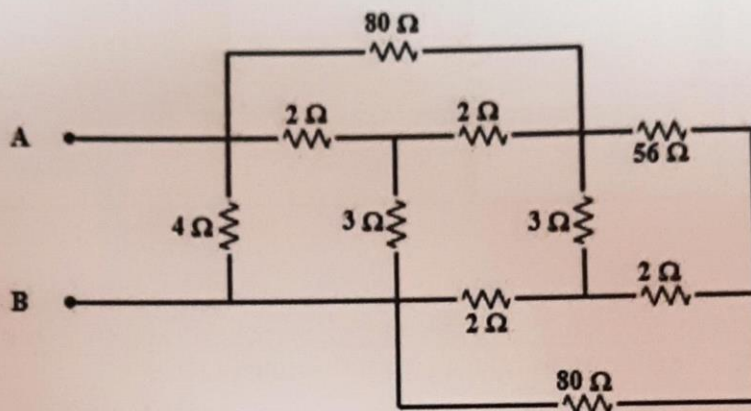


Fig. 1 A

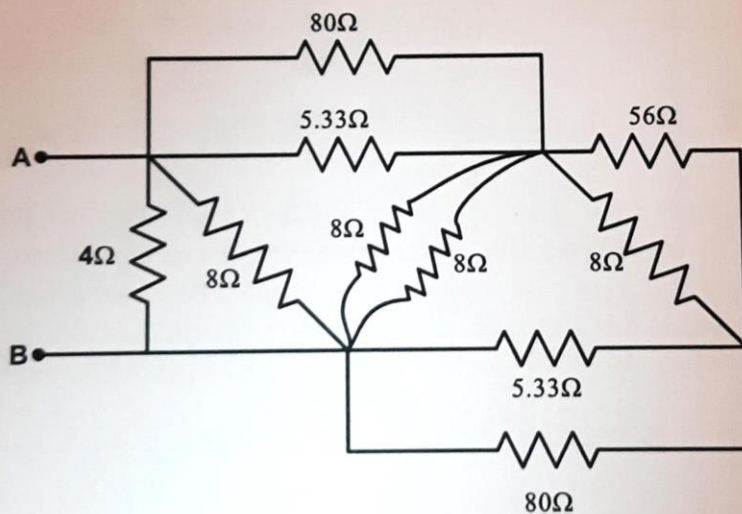

-----1M

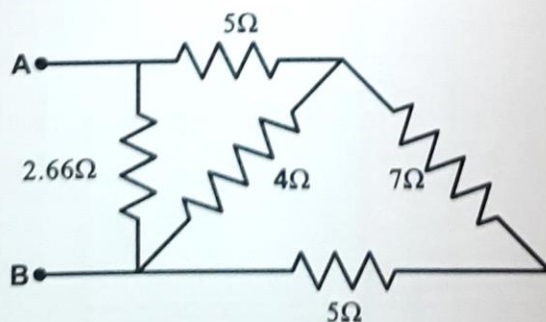


-----1M

$R_{AB} = 2\Omega$  -----1M

1 B. Realize the network defined by mesh current equations given below.

3 M

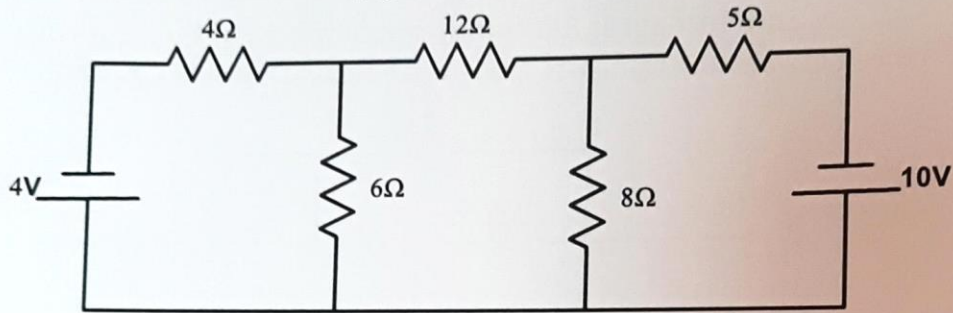
$$\begin{bmatrix} 10 & -6 & 0 \\ -6 & 26 & -8 \\ 0 & -8 & 13 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} -4 \\ 0 \\ 10 \end{bmatrix}$$



-----3M

- 1 C. In the circuit shown **Fig. 1C**, the switch is initially in position 1 for  $120 \mu s$  and then it is moved to position 2. Find the voltage across the capacitor and the charging current in the intervals (a)  $0 \leq t \leq 120 \mu s$  (b)  $t > 120 \mu s$


4 M

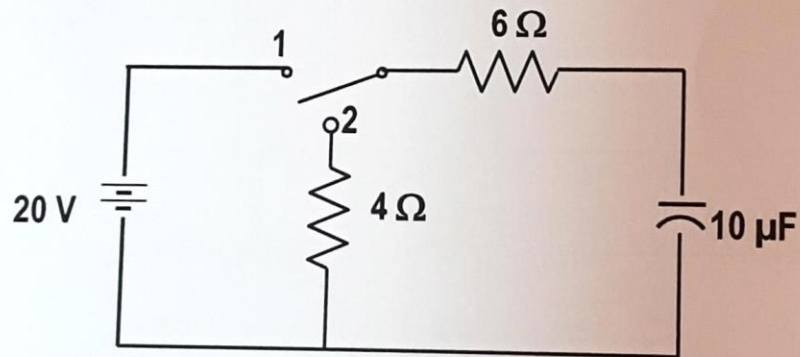

**Fig. 1C**

For time  $0 \leq t \leq 120 \mu s$ ;  $v_c = 20 \left( 1 - e^{\frac{-t}{60\mu}} \right) V$   $i_c = 3.33 \left( e^{\frac{-t}{60\mu}} \right) A$  -----2M

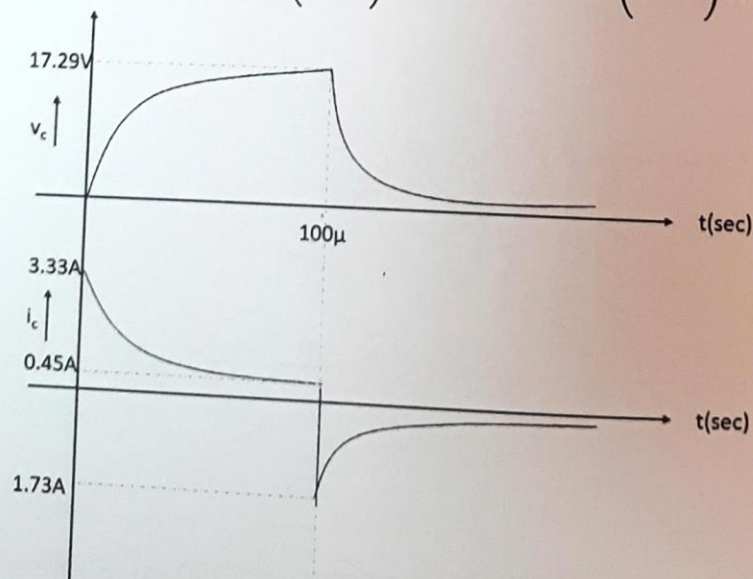For time  $t > 120 \mu s$ ;  $v_c = 17.29 \left( e^{\frac{-t'}{0.1m}} \right) V$   $i_c = -1.729 \left( e^{\frac{-t'}{0.1m}} \right) A$  -----2M





- 2 A. Find the flux density in the central limb of the magnetic core shown in the Fig. 2 A, given the current  $i = 20$  A and  $\mu_r$  of the core material = 2000. 6 M

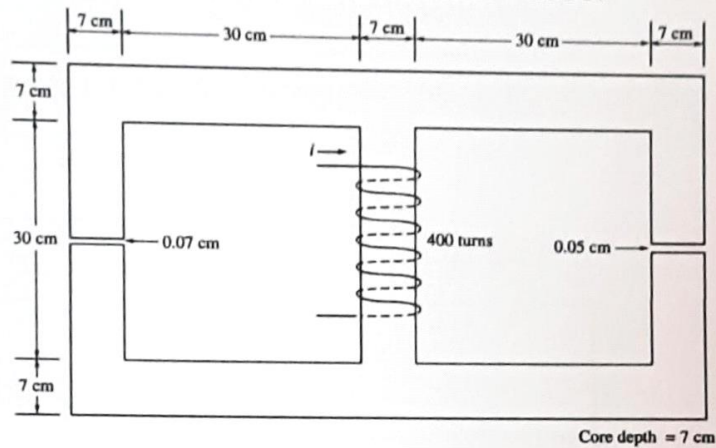


Fig. 2 A

$$S_{LEFT} = 90076.83 \text{ AT/Wb}$$

$$S_{L \text{ AIRGAP}} = 113682.102 \text{ AT/Wb} \text{-----1M}$$

$$S_{RIGHT} = 90093.066 \text{ AT/Wb}$$

$$S_{R \text{ AIRGAP}} = 81201.50 \text{ AT/Wb} \text{-----1M}$$

$$S_{CENTRAL} = 30044.56 \text{ AT/Wb} \text{-----1M}$$

$$\left. \begin{aligned} NI &= \phi_{CENTRAL} * S_{CENTRAL} + \phi_{RIGHT}(S_{RIGHT} + S_{R \text{ AIRGAP}}) \\ \phi_{LEFT}(S_{LEFT} + S_{L \text{ AIRGAP}}) &= \phi_{RIGHT}(S_{RIGHT} + S_{R \text{ AIRGAP}}) \end{aligned} \right\} \text{-----2M}$$

$$\phi_{CENTRAL} = \phi_{RIGHT} + \phi_{LEFT}$$

$$\phi_{CENTRAL} = 64.98 \text{ m Wb}$$

$$B_{CENTRAL} = 13.26 \text{ Wb/m}^2 \text{-----1M}$$

- 2 B. Three coupled coils  $L_1 = 0.4$  H,  $L_2 = 0.5$  H and  $L_3 = 0.8$  H wound on the same core as shown in the Fig. 2 B are connected in series by joining the terminals  $A_2$  to  $B_1$  and  $B_2$  to  $C_1$  and the coefficient of coupling  $k_{12} = k_{13} = k_{23} = 0.8$ . Sketch the dotted equivalent circuit of the coils connected in series and find the equivalent inductance measured across terminals  $A_1$  and  $C_2$ . 4 M


$$L_{eq} = L_1 + L_2 + L_3 + 2M_{12} - 2M_{23} - 2M_{13} \text{-----2M}$$

$$M_{12} = 0.358 \text{ H}$$

$$M_{23} = 0.506 \text{ H}$$

$$M_{31} = 0.453 \text{ H}$$
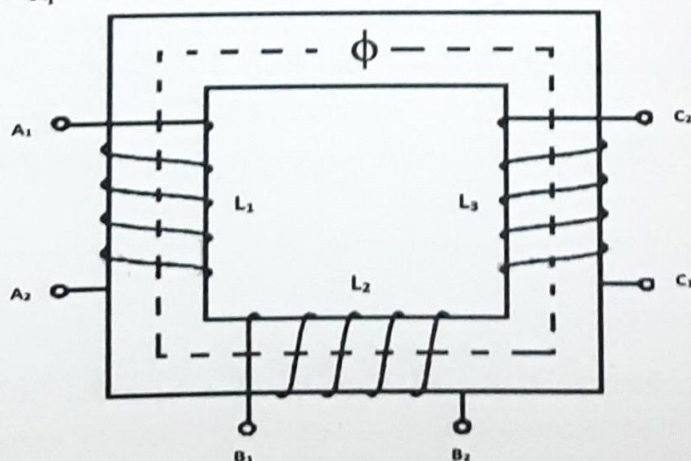
$$L_{eq} = 0.498 \text{ H} \text{-----1M}$$





- 3 A. For network shown in Fig. 3 A, calculate the value of current  $I$  and the voltage across the parallel branch. 3 M

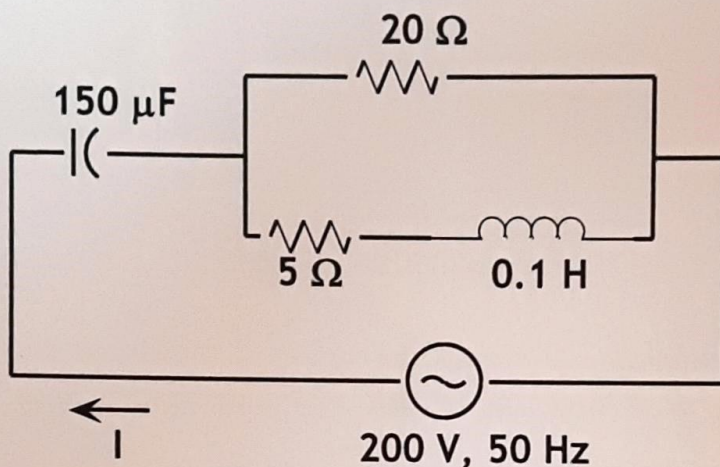


Fig. 3A

$$Z_{eq} = 19.25 \angle -44.22^\circ \Omega = 13.79 - j13.42 \Omega \text{-----1M}$$

$$I_T = 10.39 \angle +44.22^\circ \text{ A} = 7.45 + j7.25 \text{ A} \text{-----1M}$$

$$V_{parallel} = 164.64 \angle 73.68^\circ \text{ V} = 46.26 + j158.01 \text{ V} \text{-----1M}$$

- 3 B. For the network shown in Fig. 3 B, determine the impedance of the load which will dissipate maximum power, and determine the maximum power 4 M

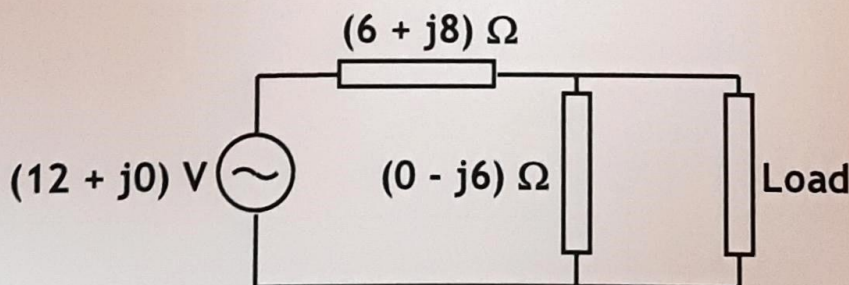


Fig. 3B

$$Z_L = Z_{TH}^* = 5.4 + j7.8 \Omega = 9.48 \angle 55.31^\circ \Omega \text{-----2M}$$

$$V_{TH} = 11.38 \angle -108.44^\circ \text{ V} = -3.6 + j10.8 \text{ V} \text{-----1M}$$

$$P_{max} = 6 \text{ W} \text{-----1M}$$

- 3 C. A parallel circuit with an RL series branch ( $R = 20 \Omega$  and  $L = 50 \text{ mH}$ ) and an RC series branch ( $R = 10 \Omega$  and  $C = 100 \mu\text{F}$ ) are connected to a variable frequency voltage source. Find at what frequency the circuit will resonate? 3 M

$$\omega_c = \frac{1}{LC} \sqrt{\frac{R_L^2 C - L}{R_C^2 C - L}} = 100000 \text{ rad/sec} = 15.915 \text{ kHz} \text{-----3M}$$



- 4 A. Three identical impedances of  $12 + j5 \Omega$  are connected in delta to a 3 phase, 3 wire, 415 V, RYB system. Taking  $V_{RY}$  as reference, find the line currents  $I_R, I_Y, I_B$  and the total power. 5 M

$$\left. \begin{aligned} V_{RY} &= 415 \angle 0^\circ V \\ V_{YB} &= 415 \angle -120^\circ V \\ V_{BR} &= 415 \angle -240^\circ V \end{aligned} \right\} \text{-----1M}$$

$$\left. \begin{aligned} I_{RY} &= 31.92 \angle -22.62^\circ A \\ I_{YB} &= 31.92 \angle -142.62^\circ A \\ I_{BR} &= 31.92 \angle 97.38^\circ A \end{aligned} \right\} \text{-----1M}$$

$$\left. \begin{aligned} I_R &= 55.29 \angle -52.62^\circ A \\ I_Y &= 55.29 \angle -172.62^\circ A \\ I_B &= 55.29 \angle 67.38^\circ A \end{aligned} \right\} \text{-----2M}$$

$$P_T = 36.685 \text{ kW} \text{-----1M}$$

- 4B. A three phase, 4 wire, 400 V, ABC system supplies a star connected load in which  $Z_A = 10 \angle 0^\circ \Omega$ ,  $Z_B = 15 \angle 30^\circ \Omega$  and  $Z_C = 10 \angle -30^\circ \Omega$ . Taking  $V_{AN}$  as reference, find the line currents & the neutral current. 5 M

$$\left. \begin{aligned} V_{AN} &= 230.94 \angle 0^\circ V \\ V_{BN} &= 230.94 \angle -120^\circ V \\ V_{CN} &= 230.94 \angle -240^\circ V \end{aligned} \right\} \text{-----1M}$$

$$\left. \begin{aligned} I_A &= 23.094 \angle 0^\circ A \\ I_B &= 15.396 \angle -150^\circ A \\ I_C &= 23.094 \angle 150^\circ A \end{aligned} \right\} \text{-----3M}$$

$$I_N = 10.94 \angle 159.4^\circ A \text{-----1M}$$

- 5 A. Discuss the role of the transformer in an electric transmission and distribution network. 4 M

Role & rating of Step up transformers at generating stations

11kV to 765 kV/400 kV/ 220 kV

Role & rating Step down transformers at subtransmission & distribution network


132 kV/ 110kV/ 66 kV/ 33 kV to 11kV

Distribution transformer 11kV to 415 V (3ph)



5 B. Explain the working principle of a three phase Induction Motor.

3 M

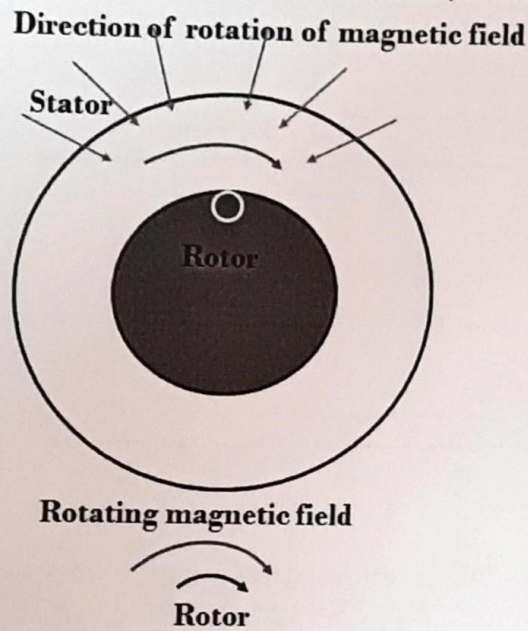

- Rotating magnetic field is cut by the rotor conductor
- EMF is induced in rotor conductor
- Current in the rotor conductor sets up a magnetic field which opposes the rotation of main field
- Main field is independent and hence rotor field tries to catch up the speed of main field to reduce the relative speed
- Rotor rotates in the same direction as that of rotating magnetic field

5 C. Sketch and explain the block diagram of a single phase digital energy meter.

3 M

